

B. TECH
(SEM II) THEORY EXAMINATION 2022-23
EMERGING DOMAIN IN ELECTRONICS ENGINEERING

Time: 3 Hours**Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A**

1. Attempt all questions in brief. **2 x 10 = 20**

- (a) Write the diode current equation of a p-n junction diode
- (b) State the application of Zener diode
- (c) Compare JFET & BJT.
- (d) Why FET is called VOLTAGE controlled device
- (e) List the ideal characteristics of op-amp.
- (f) What do you mean by IOT?
- (g) What are universal gates? Why are they called so?
- (h) What is a Logic gate? What is meant by a bit, pair, and quad?
- (i) Write a short note on MOBILE communication system.
- (j) Describe the need of modulation in communication system.

SECTION B

2. Attempt any three of the following: **10x3=30**


- (a) Draw a neat circuit diagram of HALF wave rectifier and explain its operation with output waveforms.
- (b) Explain Working Principle of Enhancement type MOSFET (n-channel). Draw its drain and transfer characteristics.
- (c) Explain how an op-amp can be used as an inverting amplifier, non-inverting amplifier and summing amplifier. Derive expressions for output voltage.
- (d) Simplify the following function using K map

$$F(A, B, C, D) = \sum m(1, 3, 4, 5, 6, 7, 9, 11, 13, 15)$$
- (e) Draw the block diagram of element of communication system. Explain functions of each block briefly.

SECTION C

3. Attempt any one part of the following: **10x1=10**

- (a) Explain the working of p-n junction diode in FB and RB conditions and draws its V-I characteristics.
- (b) Trace the output of the given circuit fig.

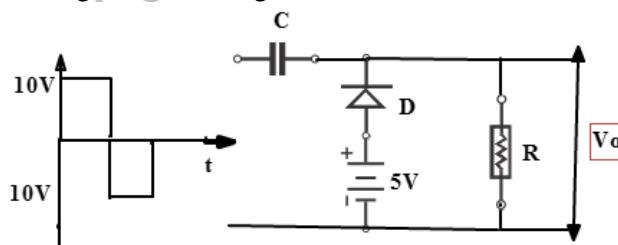


4. Attempt any one part of the following: 10x1=10

- (a) Describe the construction and working of a NPN transistor in common emitter (CE) configuration with respect to size and doping. Also, draw the input and output characteristic graph.
- (b) Draw & Explain N-channel JFET construction. Draw & Explain its characteristics.

5. Attempt any one part of the following: 10x1=10

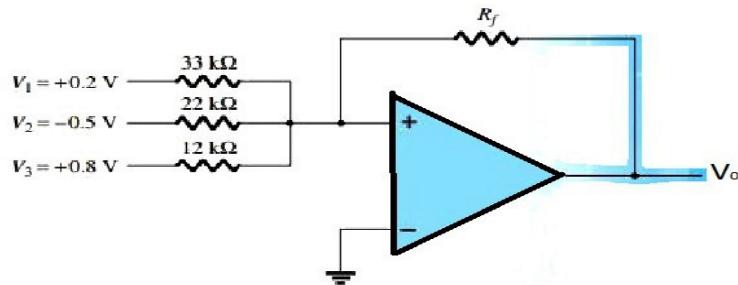- (a) Calculate the output voltage developed by the circuit of Fig. below for $R_f = 330 \text{ k}\Omega$.



- (b) Draw the Block diagram of Op-Amp and explain its each block.

6. Attempt any one part of the following: 10x1=10

- (a) Simplify the Boolean expressions to minimum number of literals
 - i) $(A + B)(A + C')(B' + C')$
 - ii) $AB + (AC)' + AB'C (AB + C)'$
 - iii) $(A+B)' (A'+B)'$
- (b) Define Universal Gates. Implement AND, OR, NOT by using NAND gates only

7. Attempt any one part of the following: 10x1=10

- (a) Define AM. Sketch the AM wave and drive the expression for AM wave.
- (b) (i) Describe briefly Satellite Communication.
(ii) Write a short note on MOBILE communication system