

B. TECH.**THEORY EXAMINATION (SEM-VI) 2016-17**
INTEGRATED CIRCUITS**Time : 3 Hours****Max. Marks : 100****Note : Be precise in your answer. In case of numerical problem assume data wherever not provided.****SECTION – A**

1. Attempt all 10 parts from the following: (2x10=20)

- a) Design a non-inverting amplifier with a gain of 2. At the maximum output voltage of 10 V and the current in the feedback resistance is 10 microampere.?
- b) Why we preferred constant current bias in op-amp?
- c) What is hysteresis voltage in Schmitt-trigger?
- d) Which type of ADC is fastest and which type having high accuracy?
- e) How the quality factor changes the frequency response of filter?
- f) How Ex-or gate work as a phase detector?
- g) Show the waveform for inverting comparator output, if input signal is $5\sin\omega t$ and reference voltage is 1V.
- h) What is sample and hold circuit, explain with diagram?
- i) If the three Mos-transistors are connected in series with different aspect ratio, calculate total aspect ratio.
- j) A second order filter has its poles at $s=-(1/2)\pm i(\sqrt{3}/2)$. The transmission is zero at $w=2$ rad/sec and is unity at $w=0$. Find the transfer function.

SECTION – B

2. Attempt any 5 parts from the following 8 parts: (10x5=50)

- a) Explain Wilson current mirror and Wildar current source with circuit diagram. Design Wildar current source for output current $10 \mu A$ and reference current is $1mA$ and $V_{cc}=15 V$ and $\beta=100$.
- b) Design IIInd order low pass filter for cut-off frequency 2 KHz.also draw the frequency response. Also Design Band –pass filter for frequencies $f_h=10$ KHz and $f_l=1$ KHz for pass-band gain 4.
- c) Find truth table and CMOS implementation of following Boolean function---
 - (i) $Y= \overline{AB} + \overline{CD}$
 - (ii) $Y= A\bar{B} + B\bar{A}$
 - (iii) $Y=A+B+C$
 - (iv) $Y=AB$
- d) Explain Half-wave precision rectifier with diagram. Design inverting Schmitt-trigger for hysteresis width 0.5 V. If $8\sin\omega t$ signal is applied to the input of this Schmitt-trigger. what are input and output waveform.
- e) i) What is resolution? Explain binary weighted DAC with diagram .
ii) Explain PLL with block diagram. What are the application of PLL.
- f) Why short circuit protection is necessary in op-amp and how many no of transistor performed this operation? And also discuss and give the expression for the DC analysis of input stage of 741 op-amp .
- g) Explain analog multiplier with circuit-diagram. Design mono-stable multi-vibrator for $100 \mu sec$ output pulse .consider $\beta=0.5$,and $V_{cc}=\pm 12V$.
- h) i) Draw the circuit diagram of triangular wave generation and explain it.
ii) Give CMOS implementation of a clocked SR flip-flop and explain its working.

SECTION – C

Attempt any 2 parts from the following 3 parts: **(15x2=30)**

- 3 What is state variable filter .Give KHN biquaid circuit and derive the expression for V_{hp} ,also derive the overall transfer function V_o/V_i , what is the condition for notch?
- 4 Explain a-stable multi-vibrator with diagram using 555 timer circuit also give the waveform. Derive the equation for time period. Design a-stable multi-vibrator for frequency 100 khz and duty cycle 50% using 555 timer circuit. What are the applications of Mono-stable multi-vibrator? What is Peak detector?
- 5 Write short notes on.
 - (i) Log and Anti-log amplifier.
 - (ii) C-MOS inverter and Slew rate.